

*National Institute of Technology Hamirpur*  
Department of Electrical Engineering  
B. Tech. (3<sup>rd</sup> Sem.) Electrical Engineering  
End Semester Theory Examination (December 2020)

EE-213  
Time: 2 hrs

Subject: Electrical and Electronic Measurements  
Maximum Marks 50


Instructions:

Each student is required to write his/her **Name, Roll No, Subject Name and Subject Code on top of first sheet** and put **Signature with Date at the bottom of each sheet** of the answer booklet.


After the examination time is over, the students may be given extra 10 minutes to scan and upload their answer booklets on Google Classroom or send back on subject teacher's Email Id. Further, delay in submission by a student may lead to deduction in marks or rejection of whole answer booklet.

**Write steps and formula used in the calculation**

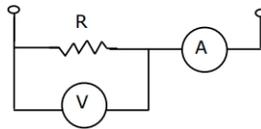- Q.1 (a)** The set-up in the figure is used to measure resistance  $R$ . The ammeter and voltmeter resistances are  $0.01\Omega$  and  $2000\Omega$ , respectively. Their readings are  $2A$  and  $180V$ , respectively, giving a measured resistance of  $90\Omega$ . Find the percentage error in the measurement.




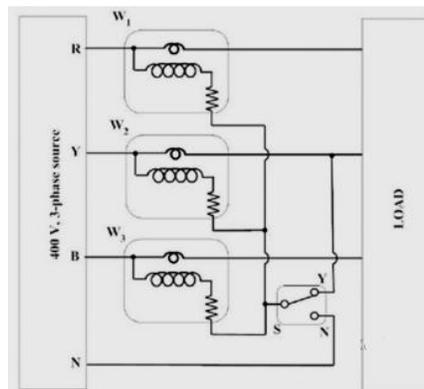- (b) Two ammeters X and Y have resistances of  $1.2\Omega$  and  $1.5\Omega$  respectively and they give full-scale deflection with  $150\text{ mA}$  and  $250\text{ mA}$  respectively. The ranges have been extended by connecting shunts so as to give full scale deflection with  $15\text{ A}$ . The ammeters along with shunts are connected in parallel and then placed in a circuit in which the total current flowing is  $15\text{ A}$ . Calculate the current in amperes indicated in ammeter X.
- (c) A  $0\text{-}1$  Ampere moving iron ammeter has an internal resistance of  $50\text{ m}\Omega$  and inductance of  $0.1\text{ mH}$ . A shunt coil is connected to extend its range to  $0\text{-}10$  Ampere for all operating frequencies. Calculate the time constant in milliseconds and resistance in  $\text{m}\Omega$  of the shunt coil respectively.
- (d) While measuring power of a three-phase balanced load by the two-wattmeter method, the readings are  $100\text{ W}$  and  $250\text{ W}$ . Calculate what will be the power factor of the load.
- (e) The load shown in the figure is supplied by a  $400\text{ V}$  (line-to-line) 3-phase source (RYB sequence). The load is balanced and inductive, drawing  $3436\text{ VA}$ . When the switch S is in position N, the three wattmeters  $W_1$ ,  $W_2$  and  $W_3$  read  $577.35\text{ W}$  each. If the switch is moved to position Y, Compute the power indicated by each watt-meters in watts.




- (f) An energy meter, having meter constant of  $1200\text{ revolutions/kWh}$ , makes  $20$  revolutions in  $30$  seconds for a constant load. Calculate the value of the load in kW.

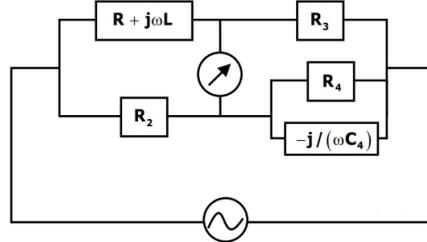- (g) A d.c. potentiometer is designed to measure up to about 2V with a slide wire of 800 mm. A standard cell of emf 1.18V obtains balance at 600 mm. A test cell is seen to obtain balance at 680 mm. Calculate the emf of the test cell.
- (h) A 500A/5A, 50 Hz current transformer has a bar primary. The secondary burden is a pure resistance of  $1\Omega$  and it draws a current of 5A. If the magnetic core requires 250 AT for magnetization, find the percentage ratio error.
- (i) The bridge shown in the figure is at balance; calculate the parameters (R and L) of the inductive coil.



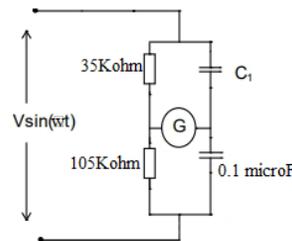
- (j) In the bridge circuit shown, the capacitors are loss free. At balance, calculate the value of capacitance  $C_1$ .



(10×3=30)

- Q.2** A watt-hour meter is calibrated to measure energy on a 250 V supply. One test a steady current of 15.0 A is passed through it for 5 hours at unity power factor. If the meter readings before and after the test are 8234.21 kWh and 8253.13 kWh respectively, calculate the percentage error. If the disc makes 290 revolutions during 5 min when a current of 20 A is passing through the meter at 250 V and 0.87 p.f., Calculate the meter constant (7)

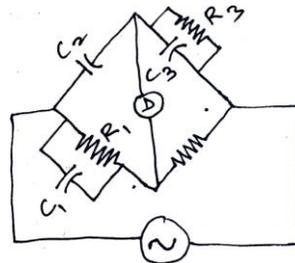- Q.3** In AC bridge as shown in Figure , determine  $C_1$  and  $R_1$  and associate loss angle, if balance is obtained at 400 Hz with  $C_2=C_3=0.01\mu\text{F}$ ,  $R_3=4\text{k}\Omega$  and  $R_4=11.5\text{k}\Omega$ . Also draw the phasor diagram of the bridge under balanced condition.



(7)

- Q.4** What are the different methods of measurement of frequency in the power frequency range. Explain the working of Ratiometer type frequency meter.

(6)