

Name of Examination: B.Tech, End Semester Theory Examination, December-2022

Branch : Electrical Engineering

Semester : Vth

Course Name : Transducer and Signal Conditioning

EE: 314

Time: 3:00 Hours

Maximum Marks: 50

Note: All questions are Compulsory. Assume suitable value for any missing data.

Question 1.


(5+5=10)

- (a) Explain the different methods used for measurement of humidity. A thermistor has a resistance of 3980 Ω at the ice point (0°C) and 794 Ω at 50°C. The resistance temperature relationship is given by $R_T = a R_0 \exp(b/T)$. (i) Calculate the constant 'a' and 'b'. (ii) Calculate the range of resistance to be measured in case the temperature varies from 40°C to 100°C.
- (b) Describe the working of Hot wire Anemometer flow meter. An electromagnetic flow meter having a flow tube of 125 mm diameter gives an output voltage of 75 mV for the magnetic flux density of 5000 V-s/cm². Determine the rate of discharge of liquid through the flow meter.

Question 2.

(5+5=10)

- (a) Show how you would use a single op amp to generate $v_0 = -\int_0^t (v_1 + 4v_2 + 10v_3) d\tau$. If the integrating capacitor is $C = 5\mu F$, determine the other component values.
- (b) Obtain v_0 of the instrumentation amplifier circuit as shown right side.

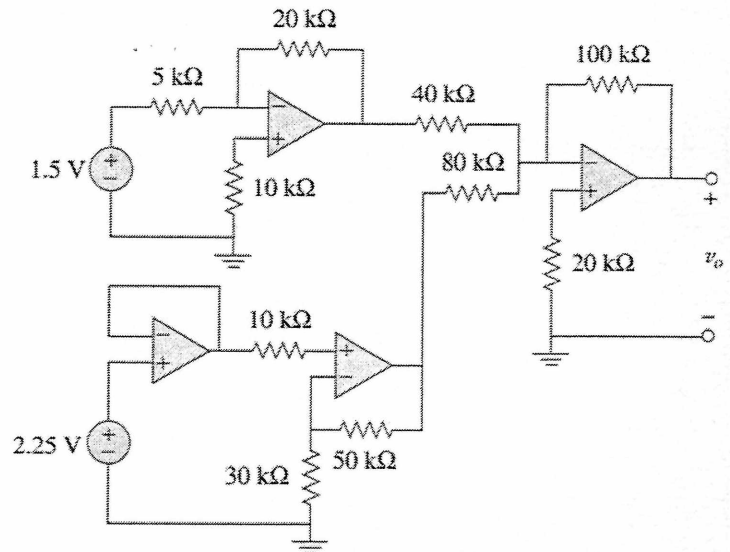

Question 3.

(5+5=10)

- (a) What is advantage of $3\frac{1}{2}$ digit display over 3 digit display? An electrically deflected CRT has a final anode voltage of 2000 V and parallel deflecting plates 1.5 cm long and 5 mm apart. If the screen is 50 cm from the centre of deflecting plates, find (a) speed of beam, and (b) deflection sensitivity of the tube.
- (b) What are the various marking mechanism used in the strip chart recorder? Also, explain the working of digital frequency meter with suitable diagram.

Question 4.

(5+5=10)

- (a) Define telemetry. Explain time division multiplexing as applied to telemetry in detail.
- (b) Define RF telemetry with an example. Explain the working of data acquisition system with suitable diagram?

Question 5.

(5+5=10)

- (a) What are the various ADC techniques? Explain the working of 4-bit flash converter with suitable diagram.
- (b) Explain the working of S/H and peak detector circuits with suitable diagram and wave form.