



इलेक्ट्रॉनिक्स एवं संचार अभियंत्रिकी विभाग
राष्ट्रीय प्रौद्योगिकी संस्थान
हमीरपुर - १७७००५ (हि.प्र.) भारत

28

EC-101 Basic Electronics Engineering

End term Examination

June, 2023

[Time Duration: 3 Hour]


Roll No.:

Max. Marks

[50 Marks]


Note: Attempt all the questions.

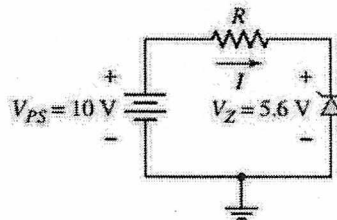1. Answer the question below in short. [5 Marks]
 - (a) At what temperature semiconductor behaves like insulators and why ?
 - (b) An p type semiconductor is electrically positive. Comment on it.
 - (c) What is Zener breakdown?
 - (d) How MOSFET is a transconductance amplifier?
 - (e) BJT is voltage or a current amplifier? justify your answer.
2. Diode is a switch. Explain by showing the working of a pn junction under different biasing conditions. Can we use it as a household switch? Comment on it. [5 Marks]
3. (a) A sample of germanium is doped to the extent on 10^{14} donor atoms/cm³ and 7×10^{13} acceptor atom/cm³. At the temperature of the sample the resistivity of pure (intrinsic) germanium is 60 Ω cm. If the applied electric field is 2V/cm, find the total conduction current density. [2.5 Marks]
(b) Find the concentration of holes and electrons in p-type silicon at 300°K if the conductivity is $100(\Omega\text{cm})^{-1}$ [2.5 Marks]
4. The resistor in the circuit shown in figure below has a value of $R = 4k\Omega$, the Zener diode breakdown voltage is $V_z = 5.6V$ and the power rating of the Zener diode is $P = 6.5mW$. Determine the maximum diode current and the maximum power supply voltage that can be applied without damaging the diode. [5 Marks]




5. Explain with the help of neat diagrams the structure of an n-channel JFET and its volt-ampere characteristics. In what ways it is different from a bipolar junction transistor? [5 Marks]
6. Mobile phone we are using is a receiver or a transmitter? Explain by showing the block diagram of a communication system with the working of each part. [5 Marks]
7. Consider the circuit in Figure below, assuming the practical diode model. Assume $V_{on} = 0.3V$ for each diode? [5 Marks]
 - (a) Sketch the output voltage waveform across R_L .
 - (b) Sketch the output voltage waveform across R_L when diode D1 is burnt in the circuit.

29

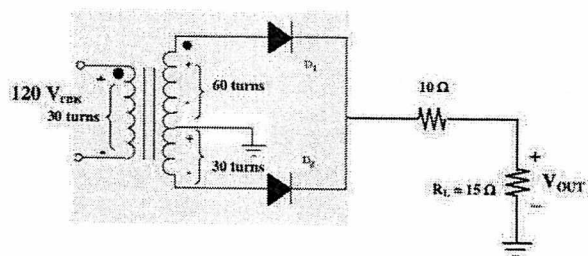


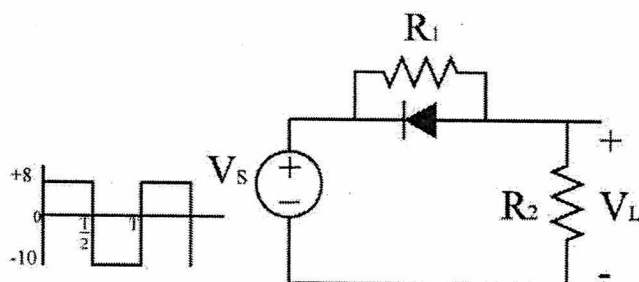8. In the circuit shown below, V_S is a square wave of period T with a maximum and minimum values of $8V$ and $-10V$ respectively. Assume that the diode is ideal and $R_1 = R_2 = 50\Omega$. Find the average value of V_L voltage?



[5 Marks]

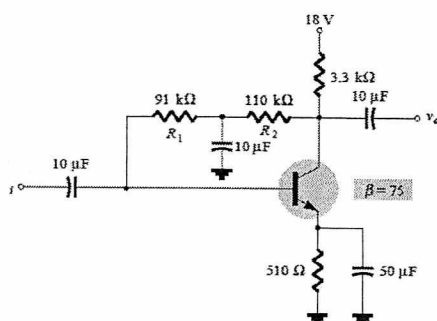9. What is biasing? Which is the best biasing technique? Derive the operating points by showing suitable diagrams. [5 Marks]
10. Determine the dc level of I_B and V_C for the network of Figure given below [5 Marks]



--- x --- x --- x ---