

Dr-R-15 Jaiel

167

8/5/2023

12

National Institute of Technology Hamirpur (HP)

[End Semester Theory Examination, May 2023]

Branch: Electrical Engineering
Subject: Power Electronics
Time: 3:00 Hours

Semester: IV
Code: EE-223
Maximum marks: 50

Note: Answer all the questions

Any missing data may be assumed suitably giving proper justification.

Q1. Write any three of the following:

[4x3]

- Explain the Principal & working of a Step Down Chopper with neat circuit diagram.
- Explain the working of the boost converter with a neat waveform and derive the peak-to-peak voltage across the capacitor.
- Explain the primary circuit and waveform and Mode of operation of the Buck-boost converter?
- Write any 04 applications of Choppers?

Q2. Write brief notes on any four of the following:

[3x4]

- How does Harmonic get created with a power electronics circuit write any two Methods of Reduction of Harmonic Content.
- Define the Total harmonic distortion?
- Explain I-V characteristics of a GTO.
- Define modulation index and its use.
- What is effect of source inductance in 1 phase rectifier circuits?

Q3. (a) What is meant by an AC Chopper?

[1]

(b) Explain briefly about a Step-up Cyclo-converter with appropriate waveform

[3]

(c) What are advantages and disadvantages of the AC voltage controller?

[3]

“OR”

(c) Explain Bridge-type Cyclo-converters with waveform

Q4. Write brief notes on any two of the following:

[3.5x2]

- Explain the Operation of SMPS.
- Integral cycle control
- Phase Angle control
- UPS

Q5. Explain the operation of any three of the following with neat diagram and waveform [3x4]

- Three-phase 180° Conduction of three-phase inverter. Also, obtain the expression for the RMS value of output voltage
- Three-phase 120° Conduction of three-phase inverter. Also, obtain the expression for the RMS value of output voltage
- What is PWM control for switching a single-phase inverter?
- What is the difference between VSI and CSI?